

ST. JOSEPH'S COLLEGE(AUTONOMOUS), BENGALURU-27  
 B.SC. ELECTRONICS- I SEMESTER  
 MID SEMESTER TEST – AUGUST 2018  
 EL118: BASIC ELECTRONICS

16-8-18

TIME :1hour

Max Marks: 30

This question paper has 2 printed pages and 3 parts.

**PART A**

Answer any 3 questions.

3x5=15


1. Explain the construction of an electrolytic capacitor and mention its merits and demerits over other types.
2. a) State and explain Kirchoff's law.  
b) What is a stiff voltage source?
3. Obtain V-I characteristics of a Silicon diode with the help of necessary diagrams and explain. Describe the phenomenon of Avalanche breakdown in the diode.
4. Explain the working of a center tapped full wave rectifier and derive its output dc voltage.

**PART-B**


Answer any 3 questions.

3x4=12

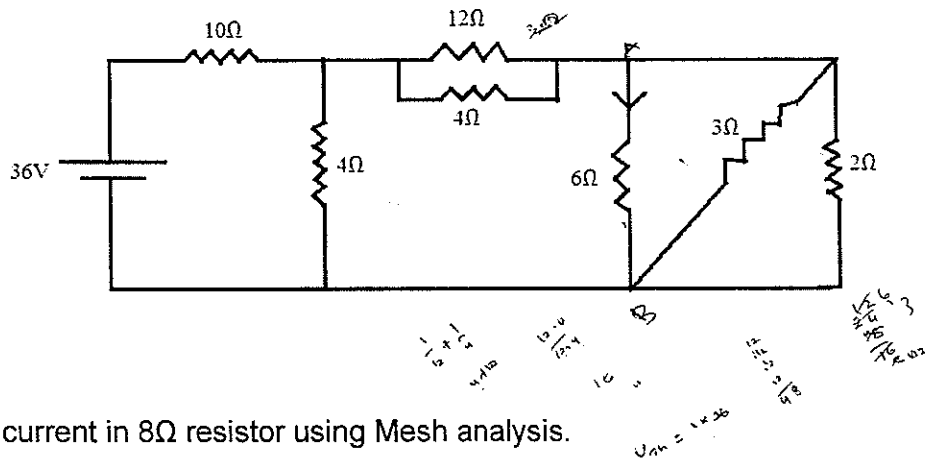5. Determine the current in  $6\Omega$  resistor.



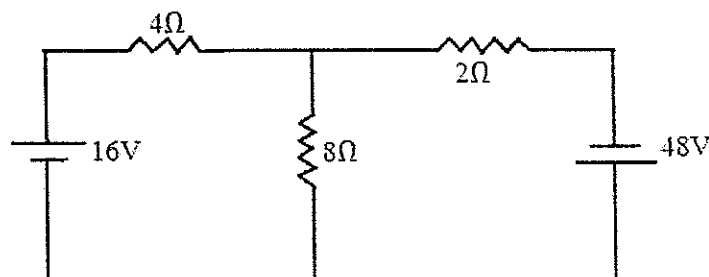6. Find current in  $8\Omega$  resistor using Mesh analysis.



$$10 \parallel 4 + 12 \parallel 4 + 3 \parallel 2$$

$$\frac{20}{4} + \frac{48}{16} + \frac{6}{5}$$

7. Determine the range of  $R_L$  for the Zener regulator to give an output of 10V.  
Given  $V_{in}=40V$ ,  $R_S=1K$ ,  $P_Z=0.25W$ .
8. A 10:1 transformer is driven by 220V, 50Hz ac voltage which is connected to a bridge rectifier circuit with 1k $\Omega$  load resistor. Determine ripple voltage and efficiency of the circuit.

**PART-C**

**Answer any 3 questions.**

**3x1=3**

9. Large value current sources are seldom found. Give reasons.
10. What is meant by linear bilateral network?
11. PIV of a diode is important while designing a rectifier. Justify?
12. Pi section filters are not used at the output of a rectifier. Substantiate.

\*\*\*\*\*