



Register Number:

DATE:

ST. JOSEPH'S COLLEGE (AUTONOMOUS), BANGALORE-27
B.Sc. ELECTRONICS – III SEMESTER
SEMESTER EXAMINATION: OCTOBER 2019
EL 318: DIGITAL ELECTRONICS

Time- 2 ½ hrs

Max Marks-70

This paper contains two printed pages and three parts

PART-A

Answer any FIVE questions.

5 × 8 = 40

- 1 a) Explain the 8421 and EXCESS-3 digital codes with examples.
b) Describe the procedure to convert grey code to binary code and vice versa. (4+4)
- 2 a) Draw the circuits of AND and NOT gates using discrete components and explain the working.
b) State and prove De Morgan's theorems using truth tables. (4+4)
- 3 a) State and explain the Duality theorem.
b) Explain NAND as universal gate. (4+4)
- 4 a) With the help of a diagram explain current sourcing in a standard TTL NAND gate.
b) Write a note on pulse characteristics and pulse duration in non ideal pulses. (4+4)
- 5 a) Write the truth table for FULL ADDER. Show how a FULL ADDER can be constructed using 2 Half Adders and an OR gate.
b) Construct 8:1 Multiplexer and describe its working. (4+4)
- 6 a) What is a decoder? Draw the logic diagram of a 3 to 8 decoder and write its truth table.
b) Write the logic diagram of a decimal to BCD encoder. (4+4)
- 7 a) Explain the working of a RS flip flop with a necessary circuit. What are the limitations of RS flip flop?
b) Differentiate between asynchronous and synchronous counters.
c) Draw the circuit of an asynchronous decade counter. (4+2+2)

PART-B

Answer any FIVE questions.

5 × 4 = 20

- 8 a) Convert the DECIMAL number 6529_{10} into equivalent OCTAL number.
b) Subtract the number $79_{(10)}$ from $25_{(10)}$ using two's complement method. (2+2)


9 Simplify the following Boolean function

$$Y = (A+B)(A+AB) + \overline{A}\overline{B} + \overline{A}\overline{C}$$

10 Simplify using K map technique and realize the logic circuit using basic gates.


$$F(A,B,C,D) = \sum m (0,1,3,9,11,12,13,15) + \sum d(2,8)$$

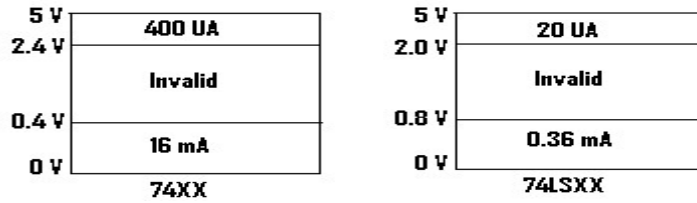11 a) Determine the fan-out when 74XX drives 74LSXX.



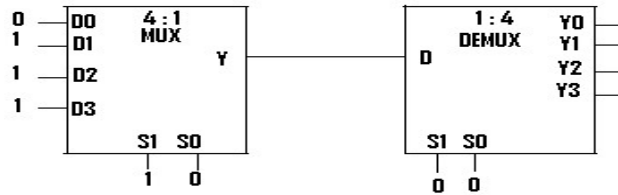b) The propagation delay time for a gate is 10 ns and power dissipation of 2mW. If 6 such gates are connected in series what is the total time delay and power dissipation of the circuit. (2+2)

12 What will be the outputs at Y and Y₀, Y₁, Y₂ and Y₃. Initially all reset.



13 Draw the circuit of a 4 bit Johnson Counter and explain its working.

14 Construct a modulo 9 ripple counter and draw its timing diagrams.

PART-C

Answer any FIVE questions.

5 × 2 = 10

15 Simplify the following Boolean expression.

$$Y = AC + C(A + A'B)$$

16 Write the Canonical form of the following

$$F(A,B,C,D) = A'BC + AD + BD' + CD' + AC' + A'B'$$

17 What is a priority encoder?

18 Draw the circuit of a two bit magnitude Comparator equality only.

19 What is the need for preset and clear inputs in a flip flop? Write their functions.

20 Draw the circuit of a CMOS inverter.

21 Identify the following ICs

IC7476, IC74150, IC7490, IC7447

-----END-----