



Register Number:

Date: 15-01-2021

ST. JOSEPH'S COLLEGE (AUTONOMOUS), BANGALORE-27

BCA –I SEMESTER

SEMESTER EXAMINATION: JANUARY 2021

CA1418: DIGITAL FUNDAMENTALS AND LOGIC DESIGN

Time- 2 1/2 hrs

Max Marks-70

PART A

Answer all the questions (10 * 2=20)

1. What are non-positional numbers? Give example.
2. What is a Logic gate? Mention any one application of logical gates.
3. Convert FACE₍₁₆₎ to its decimal equivalent.
4. Mention any two difference between sequential and Combinational circuits.
5. How is a RAM chip different from a ROM chip?
6. Design Logic circuit for X-NOR gate with truth table.
7. how JK flip flop is different from SR flip flops.
8. What is an encoder?
9. Mention the features of SRAM.
10. Simplify $x + x'y + y' + (x + y')x'y$

PART B

Answer any Five of the following questions (5 * 6=30)

11. Perform the binary operations on the following numbers

- a) 120+168
- b) 168-120
- c) 168* 120

12. Subtract 76 from 38 using two's complement method. Mention in detail the steps involved.
- 13.. Design a combination circuit for a full adder and explain it in detail.
14. With a neat block diagram explain the working of a Master Slave flip flop in detail with a mention of its truth table.
15. State and prove the two De-Morgan's theorems in detail with truth table.
16. Classify Read Only Memory and explain in detail.
17. Explain the working of four-bit synchronous counter.

SECTION C

Answer any **Two** questions.

10*2=20

18. Simplify the following Boolean function using K maps:

$$F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 9, 12) \text{ don't care conditions} = (7, 11, 15)$$

19. Design a 4:1 multiplexer and explain its functionality in detail with truth table.
20. Explain in detail the various modes of operations of registers.