



Register Number:

DATE: 15-01-2021

ST. JOSEPH'S COLLEGE (AUTONOMOUS), BANGALORE-27
B.Sc. Electronics – I SEMESTER
SEMESTER EXAMINATION -JANUARY 2021
EL 118 – BASIC ELECTRONICS

Time: 2.5 hours

Maximum marks: 70

This question paper has **THREE** printed pages and **THREE** parts.

PART – A

Answer any five of the following:

5 X 8 = 40


1. a) Obtain the phase relationship between voltage and current when a.c is applied across a series RC circuit.
b) Compare series resonance and parallel resonance. Draw frequency response graph of each case. **(4 + 4)**
2. a) Derive the charging current expression when a series RC circuit is excited by a DC source. Using the expression arrive at the definition of time constant.
b) State Kirchoff's laws for circuit analysis. **(6 + 2)**
3. a) State Thevenin's theorem.
b) State maximum power transfer theorem.
c) Draw input/ output wave form of a bridge rectifier and derive expression for the dc output voltage. **(2 + 2 + 4)**
4. a) Mention any one difference between zener breakdown and avalanche breakdown.
b) Explain with circuit diagram, the working of a voltage doubler.
c) Draw the circuit of a biased negative clipper. **(2 + 4 + 2)**
5. a) Draw the output characteristics of a CE transistor and explain how to determine output resistance and β of transistor from the characteristics curves.
b) Draw fixed bias transistor circuit with emitter resistor and arrive at expression for operating point. **(4 + 4)**
6. a) Draw r_e model circuit of a CE amplifier with voltage divider bias and obtain expression for Z_i , Z_o , A_i , and A_v .
b) Draw the circuit of a CC amplifier. Why CC amplifier is called a buffer amplifier? **(6 + 2)**
7. a) Draw typical drain characteristics and transfer characteristics of JFET.
b) Draw the construction diagram of enhancement type MOSFET.
c) Draw circuit diagram of a CMOS inverter.
d) Compare CE and CB amplifiers with respect to input and output resistances. **(2 + 2 + 2 + 2)**

PART – B


Answer any five of the following:

5 X 4 = 20

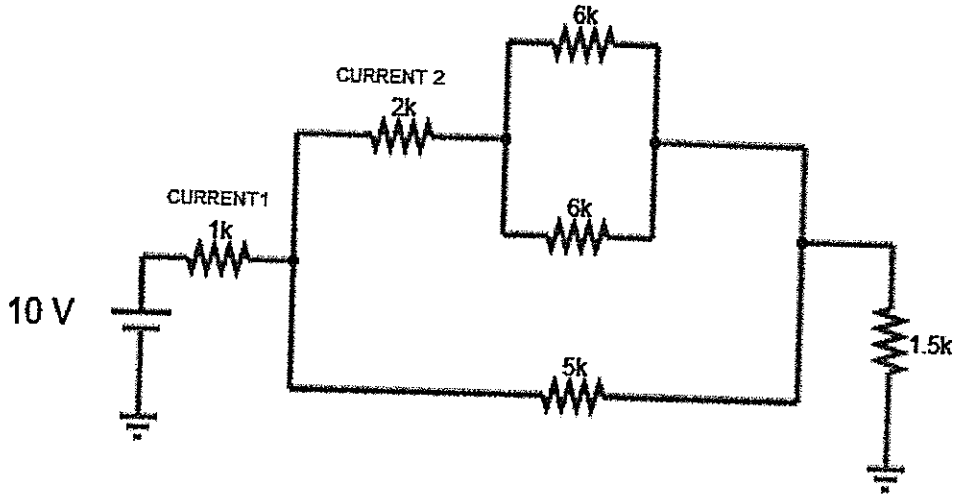8. A coil having resistance of 120Ω and inductance 36 H is connected across a 12 V battery. Find (i) time constant of the circuit (ii) current after 0.3 seconds (iii) current after 1.5 seconds.
9. Calculate the total resistance across the voltage source and current 1 and current 2 in the circuit below.




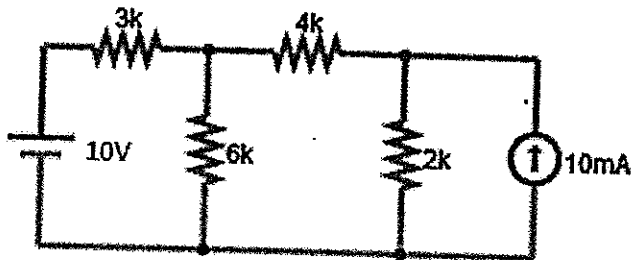10. Nortonise the following circuit assuming the 4 k resistor as the load.



11. Design a zener regulator for the following specifications:
 - (i) Output voltage is 5 V
 - (ii) Load current = 20 mA
 - (iii) Zener power dissipation = 500 mW
 - (iv) Input voltage = $12 \pm 3 \text{ V}$
12. A half wave rectifier uses a transformer of turns ratio $0:1$. The AC input is 230 V , 50 Hz . Calculate the dc output voltage and current if the load resistance is $1 \text{ k}\Omega$. Also calculate the efficiency of the rectifier. Assume that the diode used is ideal.
13. The data sheet of a n-channel FET reveals that $I_{DSS} = 12 \text{ mA}$, and $V_{GS(OFF)} = -6 \text{ V}$. Draw its transfer characteristics.

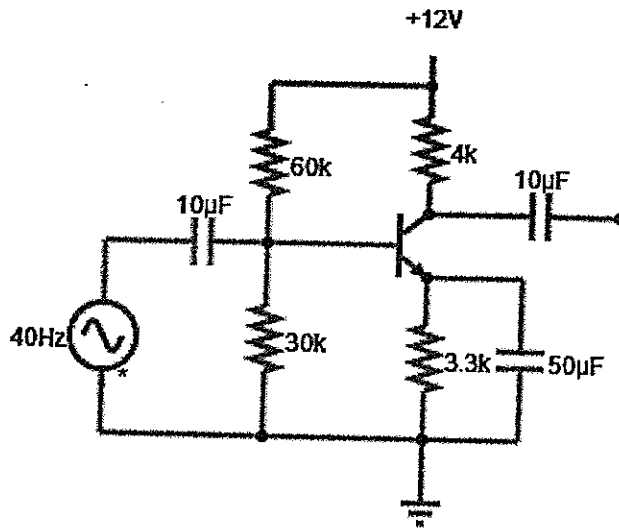14. Calculate the voltage gain of the amplifier shown below. β of the transistor is 120.




PART-C

Answer any five of the following

5 x 2 = 10

15. Two resistors of same colour code (RED, RED, BLACK, SILVER) are connected parallel to each other. What is the effective resistance if tolerance is neglected?

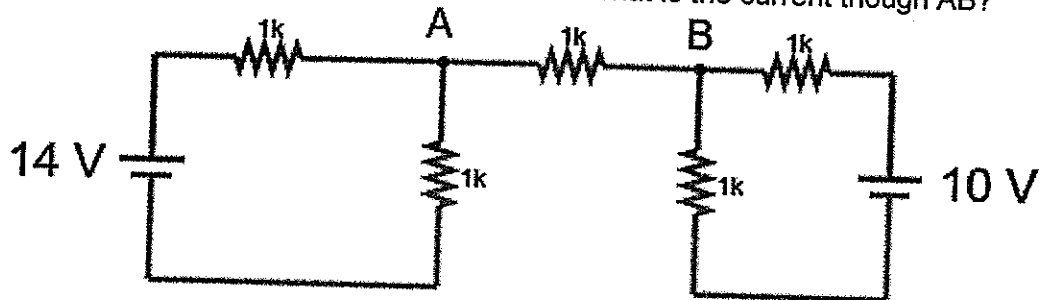16. Is there a potential difference between A and B? What is the current through AB?



17. Compare the collector voltage in a base bias transistor if the base resistor is (i) shorted (ii) opened.

18. Can we interchange L and C in the LC filter of a rectifier? Justify your answer.

19. What is the use of emitter bypass capacitor in a CE amplifier circuit?

20. Draw schematic diagram of a 7 segment LED display.

21. Represent impedance $6+j8$ in polar form.

XXXXXXXXXXXXXXXXXXXXXXXXXXXX